

## How DP instructions affect Flags C, V, Z, N

Instructions	Effect on Flags		
	if S-bit = 0	if S-bit = 1 and no shift/rotate	if S-bit = 1 and shift/rotate is there
add, sub, rsb, adc, sbc, rsc	No flags are affected	All 4 flags are affected, ALU carry is used	
cmp, cmn	All 4 flags are affected, ALU carry is used		
and, orr, xor, bic, mov, mvn	No flags are affected	Only Z and N are affected	C, Z and N are affected shift/rotate carry is used
tst, teq	Only Z and N are affected		

## Circuit for maintaining Flags

This circuit will, of course, have an edge triggered 4-bit register (or 4 edge triggered flip-flops) that will be set according to the table shown above. The inputs required for it are as follows.

- Whether it is a DP instruction? If yes, which of the 16 instructions it is or to which of the 4 sub-classes of DP instructions (as per the rows of the above table) it belongs?
- S-bit of the instruction.
- Whether shift/rotate for operand 2 is specified or not? No shift/rotate is encoded as LSL #0. Other three types of shifts with #0 (i.e., LSR #0, ASR #0 and ROR #0) are used for some special purpose and are out of scope for the current Lab assignment.
- Carry output from ALU.
- Carry output from shifter.
- Result output from ALU (for determining next value of Z and N flags).
- MSB's of ALU operands (for determining next value of V flag).

## Determining the next value of V flag

Let us use the following notation.

$A_{31}$  and  $B_{31}$  are the msb's of the ALU operands

$S_{31}$  is the msb of the result produced by ALU

$C_{32}$  and  $C_{31}$  are the final and per-final carries from ALU

If both  $C_{32}$  and  $C_{31}$  are available, the simplest way to determine overflow is as follows.

$$V = C_{31} \text{ xor } C_{32} \quad [1]$$

However, since we are using + operator of VHDL rather than doing bit-by-bit addition,  $C_{31}$  is not available to us. We can determine overflow by looking at the signs of operands and result, as shown below (assuming add operation being performed by ALU).

$$V = A_{31}.B_{31}.S_{31}' + A_{31}'.B_{31}'.S_{31} \quad [2]$$

Alternatively, we can first determine  $C_{31}$  as shown below and then apply equation [1].

$$\text{Since } S_{31} = A_{31} \text{ xor } B_{31} \text{ xor } C_{31}, \text{ we get } C_{31} = A_{31} \text{ xor } B_{31} \text{ xor } S_{31} \quad [3]$$

Note that while equation [1] does not depend on whether the operation being performed by ALU is addition or subtraction, equations [2] and [3] assume the operation to be add operation. In case of subtract operation, we need to replace  $B_{31}$  by  $B_{31}'$  and in case of reverse subtract operation, we need to replace  $A_{31}$  by  $A_{31}'$ .